

Infrared Communication

Christopher Houle

Christopher Wilson

May 1, 2008

University of Maine

ECE 403 Final Report

i. Abstract

A infrared transmission and reception system was designed and built with the original specifications requiring a transmission speed of 9600 bits per second, a transmission distance of 10 feet, and a string length of 10 characters. An oscillator and NAND gate were used for mixing the signal in the transmitter. Various filters, an amplifier, and a Schmitt Trigger were used to reconstruct the signal at the receiver. A final transmission speed of 19200 bits per second at a distance of 14 feet of an unlimited string length were achieved. The transmission speed is in the middle of the standard baud rates and the transmission distance is on par with commercial devices using infrared technology.

ii. Table of Contents

Introduction.....	1
Breakdown.....	2
Transmitter.....	2
Receiver.....	4
Details.....	6
Transmitter Hardware.....	6
5 Volt Supply.....	6
Stage 1: Wien-Bridge Oscillator.....	6
Stage 2: Schmitt Trigger.....	8
Stage 4: NAND Gate.....	9
Stage 5: Transmission Circuit.....	9
Simulation of the Transmitter Hardware.....	10
Receiver Hardware.....	11
5 Volt Supply.....	11
Stage 6: Receiver Diode and Transimpedance Amplifier.....	11
Stage 7: Bandpass Filter.....	11
Stage 8: Amplifier Network.....	12
Stage 9: Schmitt Trigger and Rectifier.....	12
Simulation and Testing of Receiver Hardware.....	12
Transmitter Software.....	13
Receiver Software.....	14
Testing.....	15
Results.....	16
Project Issues.....	17
Project Improvements.....	17
Appendix.....	19
Appendix A: Project Proposal.....	19
Appendix B: Transmitter Complete Schematic.....	20
Appendix C: Transmitter Simulation.....	21
Appendix D: Receiver Complete Schematic.....	23
Appendix E: Operating Instructions.....	24
Appendix F: References.....	25
Appendix G: Parts List.....	26
Appendix H: Data Sheets.....	27

iii. List of Figures, Tables, Graphs, and Equations

Figures:

Figure 1: Block Diagrams.....	2
Figure 2: Software Flowcharts.....	5
Figure 3: Wien-Bridge Oscillator.....	7
Figure 4: Inverting Schmitt Trigger.....	8
Figure 5: Transmission Circuit.....	9
Figure 6: Desired and Actual Examples of Input Patterns.....	15

Tables:

Table 1: Comparison of Specifications and Results.....	17
--	----

Graphs:

Graph 1: AC analysis of Bandpass and Amplifier Stages.....	13
Graph C.1: AC analysis of Bandpass and Amplifier Stages.....	21
Graph C.2: AC analysis of Bandpass and Amplifier Stages.....	22

Equations:

Equation 1: Transfer Function of Wien-Bridge Oscillator.....	7
Equation 2: Oscillation Frequency of Wien Bridge Oscillator.....	7
Equation 3: Gain of Wien-Bridge Oscillator.....	8
Equation 4: Calculating the Value of R3 Resistor.....	8
Equation 5: Schmitt Trigger Nodal Analysis.....	9
Equation 6: Reorganized Version of Equation 5.....	9
Equation 7: Diode Current.....	10
Equation 8: Transimpedance Amplifier Gain.....	11
Equation 9: Bandpass Filter Frequency.....	11
Equation 10: Amplifier Gain.....	12